

數位系統設計實習

Lecture 4

CLA/Sequential Logic

指導老師：陳勇志 教授
實習課助教：黃柏皓

Outline

2

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3

Chapter

3

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3

Recap Behavior Modeling

4

□ Gate-level Modeling :

- 每個指令輸出只能1個位元

*信號必須是`wire`資料型態

*例如

```
xor g1(sum, A, B);
```

```
and g2(carry, A, B);
```

□ Dataflow Modeling :

- 資料流敘述的前後次序不重要。

*出現在 `=` 敘述左邊的信號必須是`wire`資料型態

*例如 `assign out = A + B;`

□ Behavior Modeling :

- `always`方塊內敘述的前後次序很重要。

*出現在 `=` 敘述左邊的信號必須宣告`reg`資料型態

例如 `always@ (A, B) //always@()`

```
out = A + B;
```

*可以用行為來描述電路

*例如 `if`、`elseif`、`case`、`for loop`……等

Recap Behavior Modeling

□ Initial Statement :

- 從時間 0 開始

- *只執行一次

- *通常用於初始化、監控、波形

- *多個 **Initial block** 會並發執行

- *必須將多個行為語句分組，通常使用關鍵字 **begin** 和 **end**

□ Always Statement :

- 從時間 0 開始

- *以循環方式連續執行always區塊中的語句

- *用於對數位電路中連續重複的活動區塊進行建模

- *必須將多個行為語句分組，通常使用關鍵字 **begin** 和 **end**


Recap Behavior Modeling

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```




Chapter

7

- Verilog 複習 : Behavior-Level
- **4-bit Carry Look-ahead Adder**
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3

4-bit Carry Look-ahead Adder

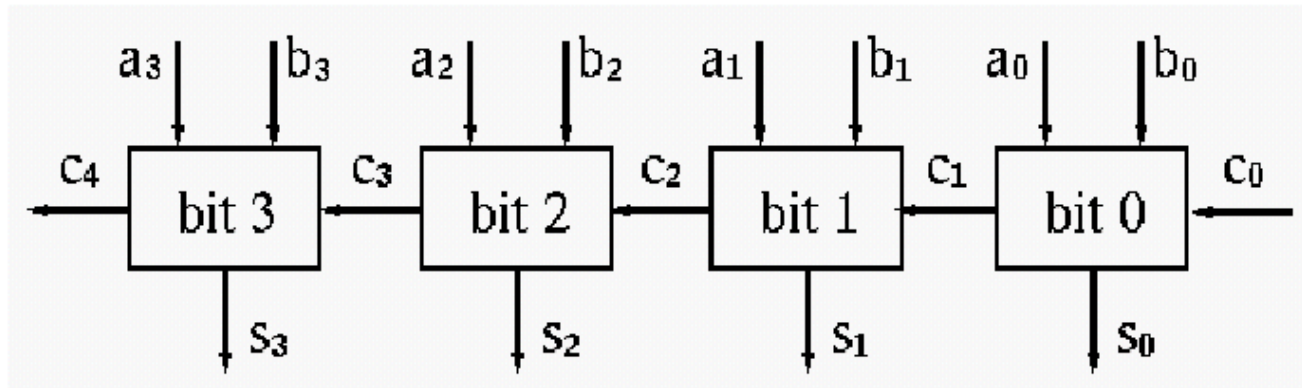
- 傳統的 ripple carry adder 在做加法時須要等上一級的 carry out 產生後才能繼續下去，對於 16-bit adder，甚至於 n -bits adder 所造成嚴重之 delay。




Ripple Carry Adder

- CLA 就是針對改善 delay 而設計出來的架構，其想法是希望將所有的進位一次運算完成。

4-bit CLA

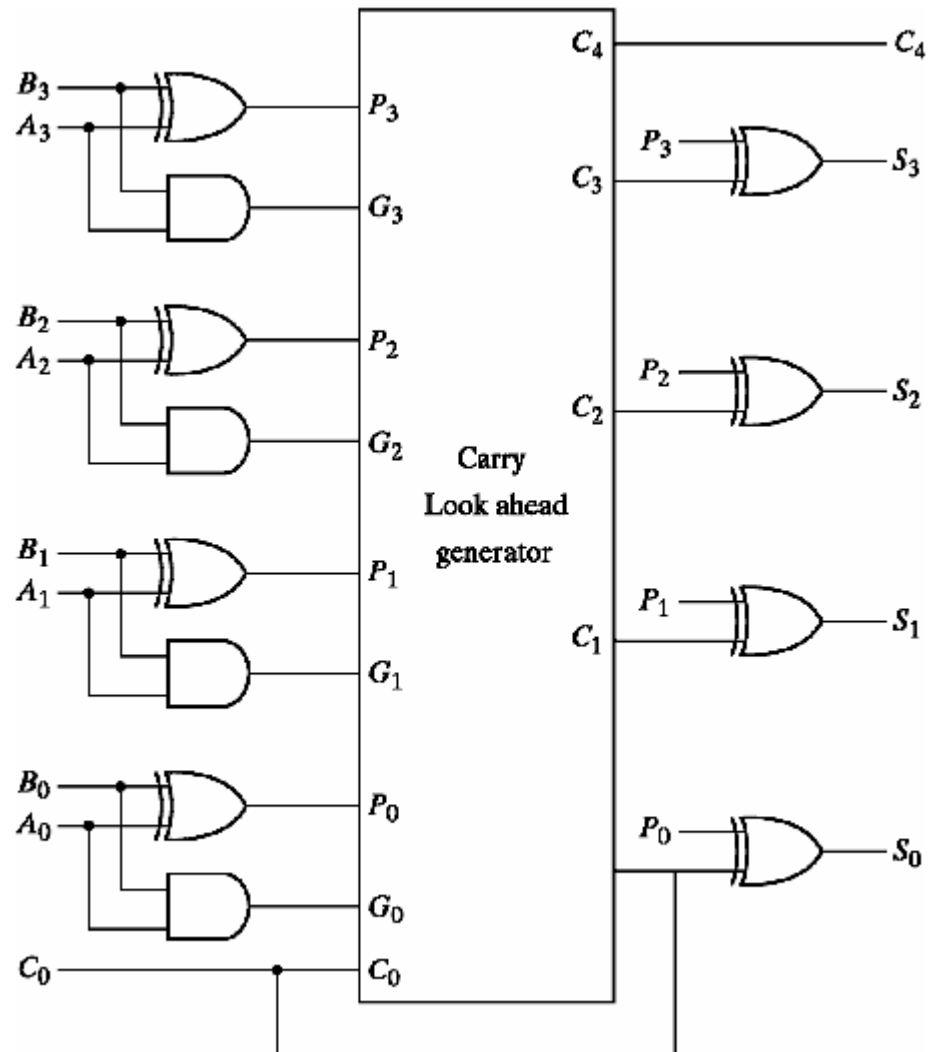

4-bit CLA

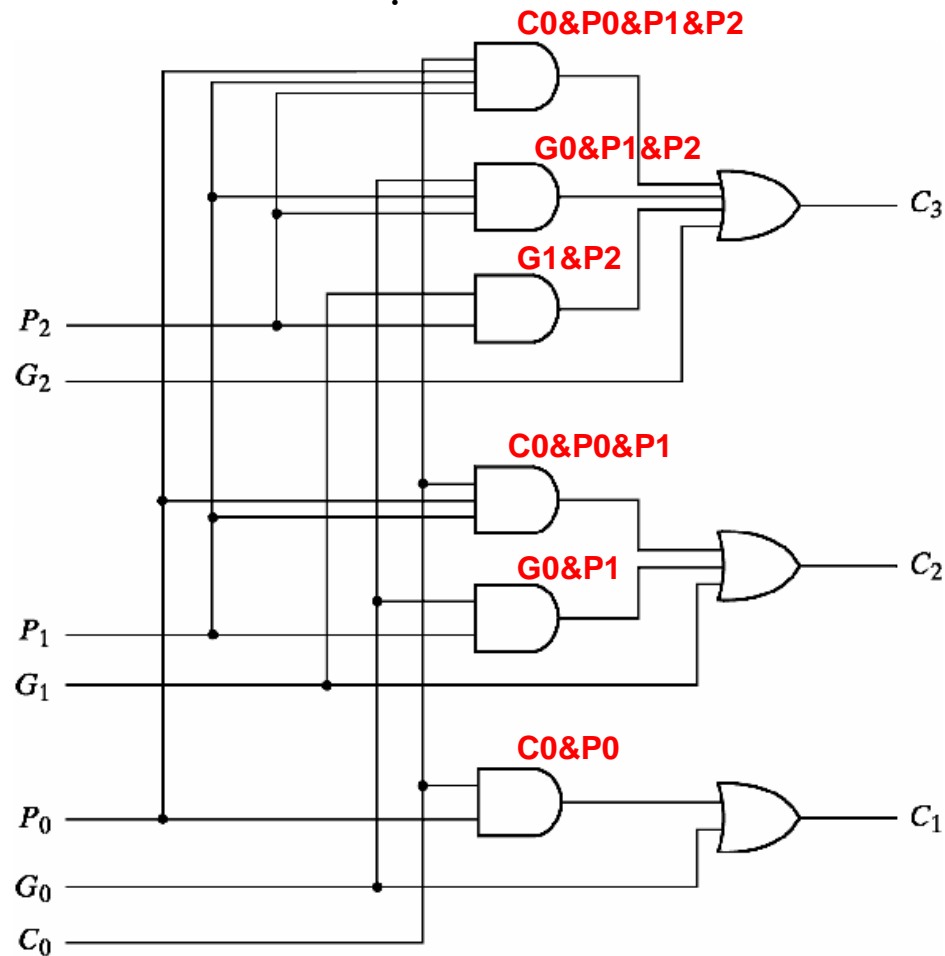

Carry Look-ahead Generator

Chapter

11

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- **Sequential Logic**
- Latch and Flip-flop
- LAB 4-1 ~ 4-3


Sequential Logic

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



Sequential Logic

Blocking vs. Nonblocking :

Blocking (=), 具有順序性, 敘述會與先後有關係 (順序處理)

Non-Blocking (<=), 具有同時性, 敘述與先後沒有關係 (平行處理)


Blocking :

```
a = in;
```

```
b = a;
```

```
c = b;
```

```
//in=a=b=c
```

 


Nonblocking :

```
a <= in;
```

```
b <= a;
```

```
c <= b;
```

 

Sequential Logic

Blocking vs. Nonblocking :

```
input In;
reg [3:0] A, B, C;

always @( posedge CLK ) begin

    /* Blocking */           // 有順序執行，同C概念
    A[0] = In;               // 1CLK後A[0] = In
    A[1] = A[0];             // 1CLK後A[1] = A[0] = In
    A[2] = A[1];             // 1CLK後A[2] = A[1] = A[0] = In
    A[3] = A[2];             // 1CLK後A[3] = A[2] = A[1] = A[0] = In

    /* Non-Blocking */       // 同時執行，此範例有資料平移的效果
    B[0] <= In;               // 1CLK後B[0]存進In, B[1]存進B[0](存In之前的值)
    B[1] <= B[0];             // 2CLK後B[1]存進In
    B[2] <= B[1];             // 3CLK後B[2]存進In
    B[3] <= B[2];             // 4CLK後B[3]存進In
```

Chapter

15


- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- **Latch and Flip-flop**
- LAB 4-1 ~ 4-3

Latch and Flip-flop

- Latch 與 Flip-flop 均是數位電路中可以提供位元狀態儲存的裝置，它可以將邏輯狀態「0」或「1」存放在裝置內直到位元值需要改變或電源被切除。
- 由於有兩個穩定的輸出狀態，所以被稱為雙穩態電路。

Latch and Flip-flop

□ D latch :

 

(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	$Q = 0$; Reset state
1	1	$Q = 1$; Set state

(b) Function table



Latch and Flip-flop

- D latch :

```
module D_latch(D, control, Q);  
input D, control;  
output Q; //output reg Q;  
reg Q;  
always @(control or D)  
if (control) Q = D;  
endmodule
```

Latch and Flip-flop

- Master-slave D Flip-flop :

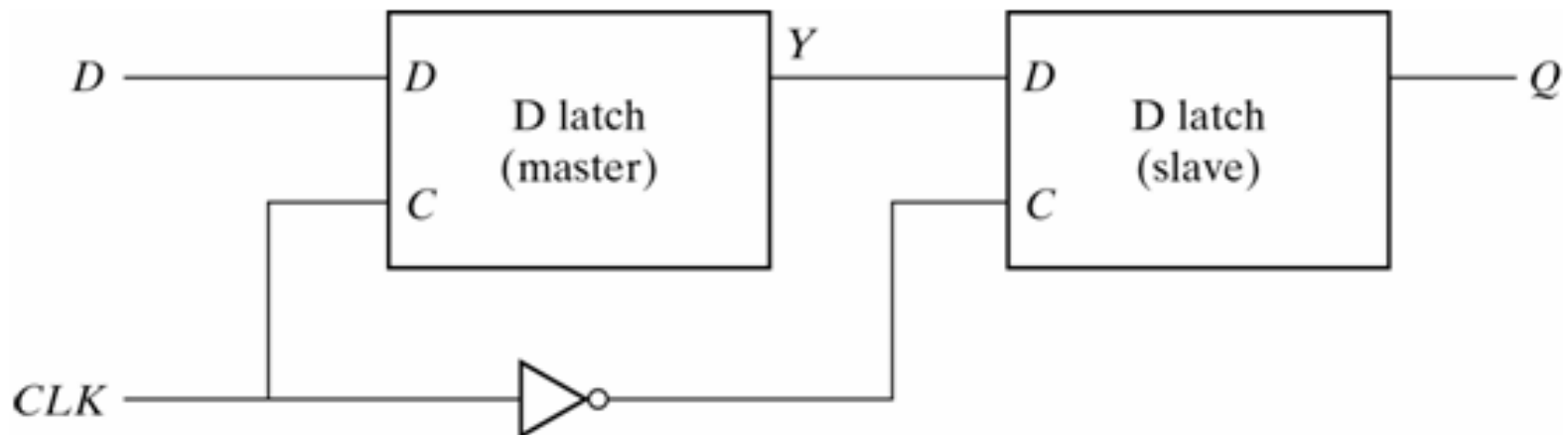 

Latch and Flip-flop

- Characteristic Table of D Flip-flop :

D_{\leftarrow}	$Q(t+1)_{\leftarrow}$	
0_{\leftarrow}	0	(Reset) $_{\leftarrow}$
1_{\leftarrow}	1	(Set) $_{\leftarrow}$


Latch and Flip-flop

- D Flip-flop :


```
module D_FF (D, CLK, Q);  
input D, CLK;  
output Q; //output reg Q;  
reg Q;  
always @(negedge CLK)  
    Q <= D; //Q = D;  
endmodule
```

Latch and Flip-flop

□ JK Flip-flop

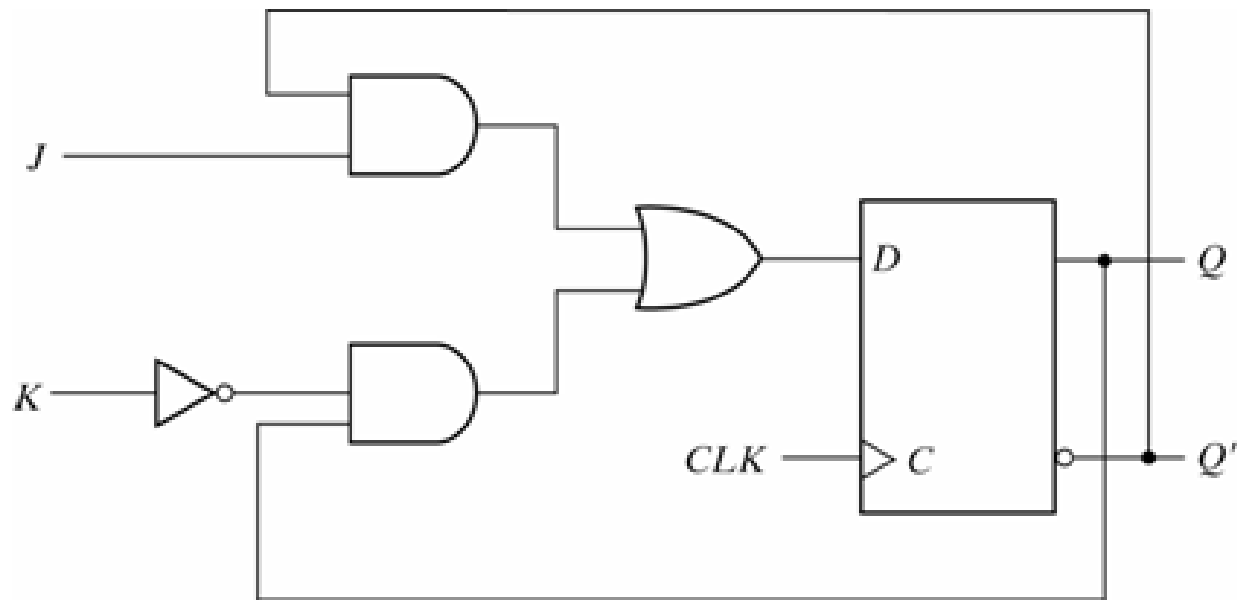


(a) Circuit diagram

 

(b) Graphic symbol

Latch and Flip-flop

 

JK Flip-flop 之時序圖


Latch and Flip-flop

- Characteristic Table of JK Flip-flop :


J_{\downarrow}	K_{\downarrow}	$Q(t+1)_{\downarrow}$
0 _↓	0 _↓	$Q(t)$ (No change) _↓
0 _↓	1 _↓	0 (Reset) _↓
1 _↓	0 _↓	1 (Set) _↓
1 _↓	1 _↓	$Q'(t)$ (Complement) _↓

Latch and Flip-flop


□ T Flip-flop :

 

(a) From JK flip-flop

 


(b) From D flip-flop

 

(c) Graphic symbol

Latch and Flip-flop

 

T_{\leftarrow}	$Q(t+1)_{\leftarrow}$
0_{\leftarrow}	$Q(t)$ (No change) _{\leftarrow}
1_{\leftarrow}	$Q'(t)$ (Complement) _{\leftarrow}

Characteristic Table of T Flip-flop

Chapter

27

- Verilog 複習 : Behavior-Level
- 4-bit Carry Look-ahead Adder
- Sequential Logic
- Latch and Flip-flop
- LAB 4-1 ~ 4-3


LAB 4-1

- 4-bit Carry Look-ahead Adder， $A[3:0]$ 、 $B[3:0]$ 及 $C0$ 為輸入，輸出為 $S[3:0]$ 及 $C4$ ，請使用Verilog HDL描寫出，並於Quartus II模擬訊號波型加以驗證結果。

```
input [3:0]A,B;  
input C0;  
output [3:0]S;  
output C4;
```

29

- $\{C4, S\}$

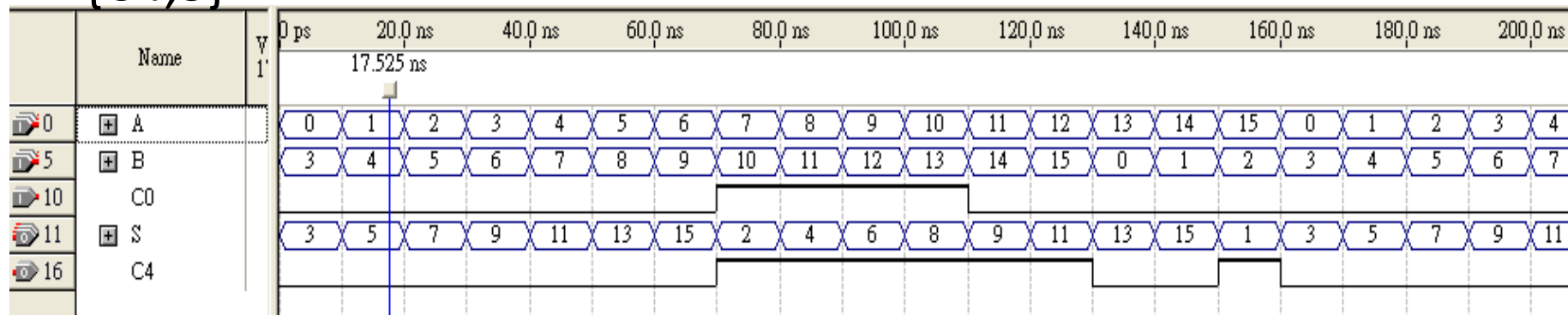


LAB 4-2

- 請寫出含有set及reset之JK正反器(負緣觸發、以behavior方式描述，set與reset跟隨clk動作，set與reset都是等於1時動作)。

JK正反器

31

? 課堂檢查

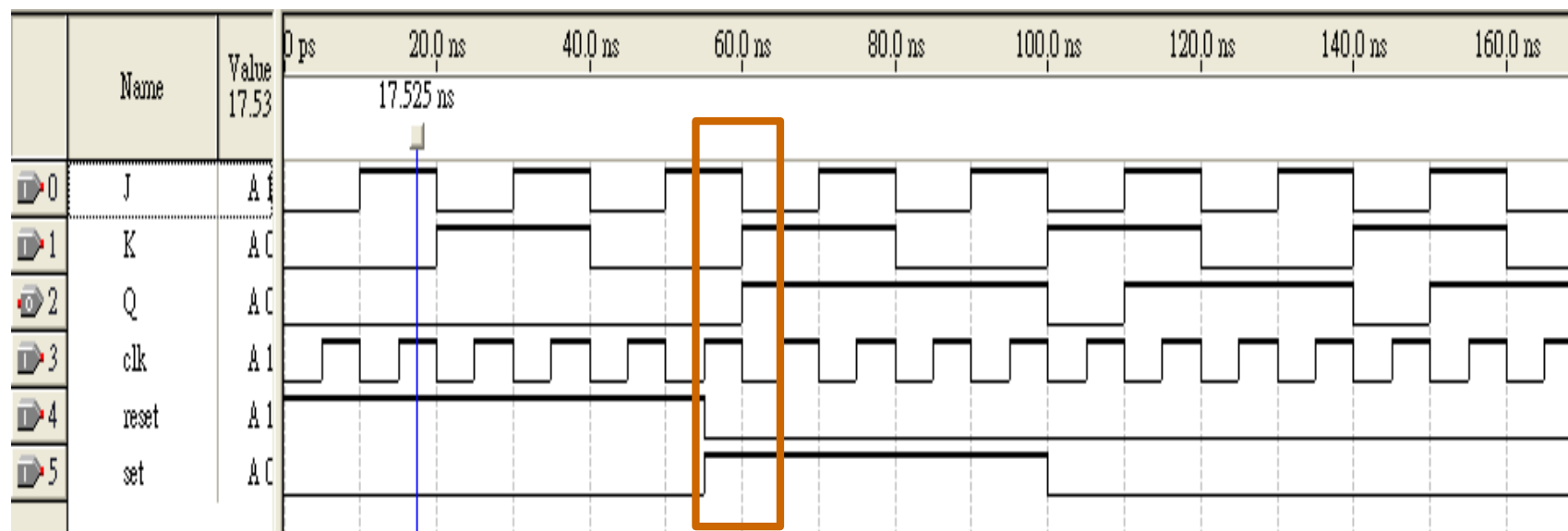


LAB 4-3

- 使用 Verilog HDL 設計一個4位元具有平行輸入之暫存器，其輸入為D_in[3:0], clk, rst, load, 輸出為D_out [3:0]（clk為正緣觸發）。

4位元平行輸入之暫存器

33

? 課堂檢查

 

LAB4

34

下課前將各Lab繳交至moodle：

上傳verilog.v

波形截圖